

Inverter Paper Circuit

Inverts the input signal.

$$V_{out} = -V_{in}$$

Recommended values:
R#: 10k Ω

