
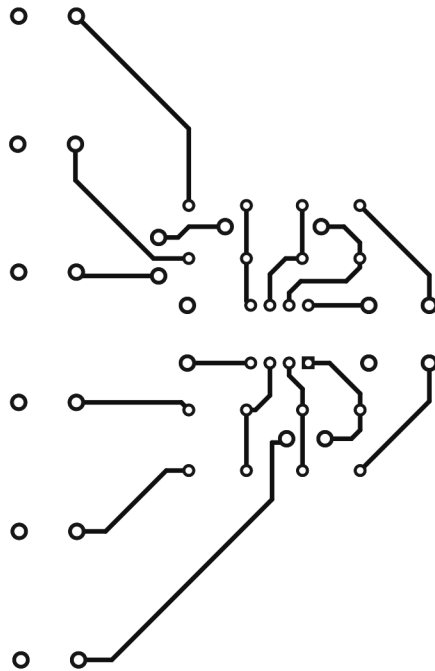


SUM

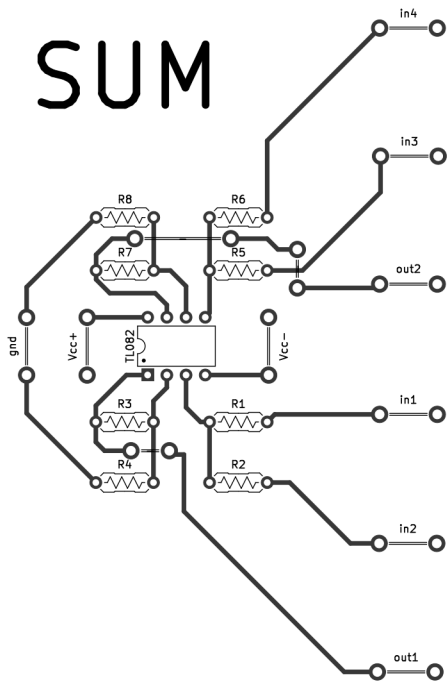


Summation Paper Circuit

Sums two signals' voltage.


$$V_{out} = V_1 + V_2$$

Recommended values:

R#: 10kΩ

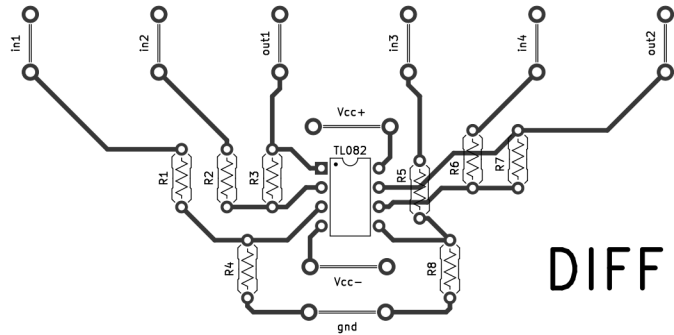

DIFF

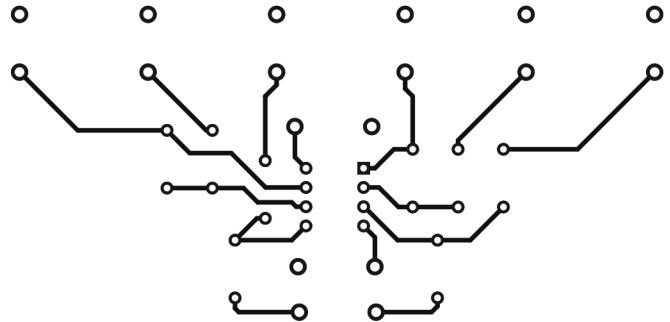

Differential Paper Circuit

Takes the difference of two signals' voltage.

$$V_{out} = V_1 - V_2$$

Recommended values:

R#: 10kΩ